

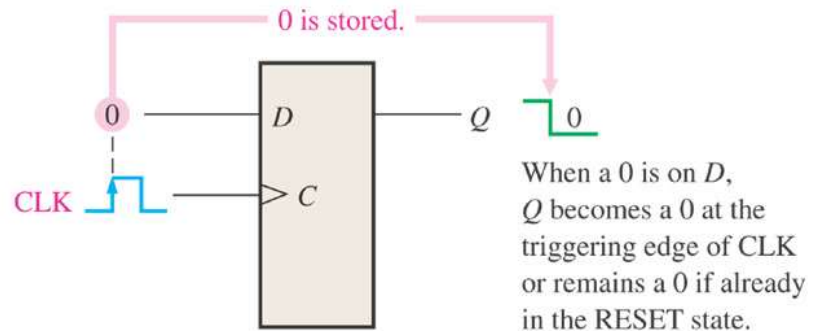


Chapter 9 Shift Register


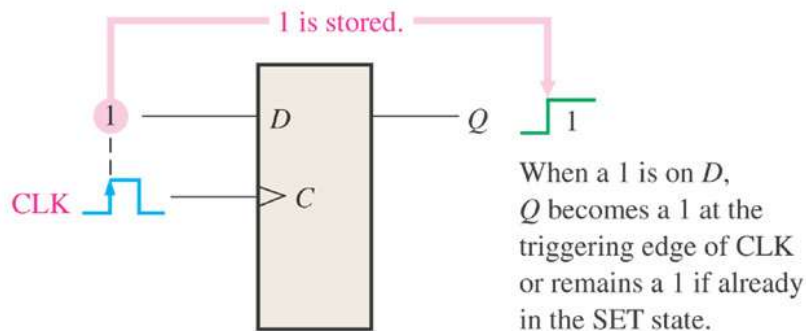
9.0 Registers

- One or more flip-flops used to store and shift data



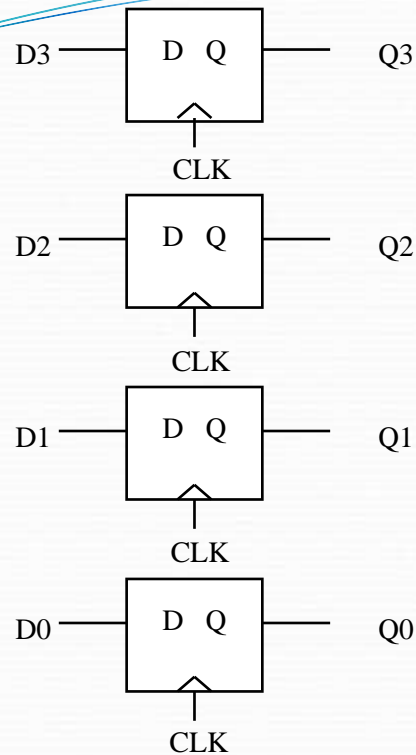

A 4-Bit Register

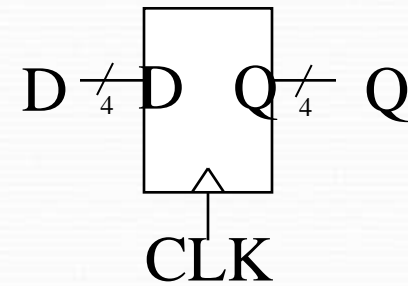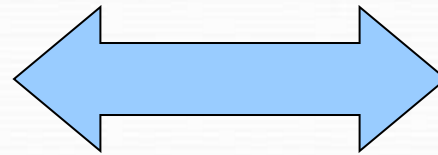

Could be called a parallel-in/parallel-out register.

9.1 Basic Shift Register Functions


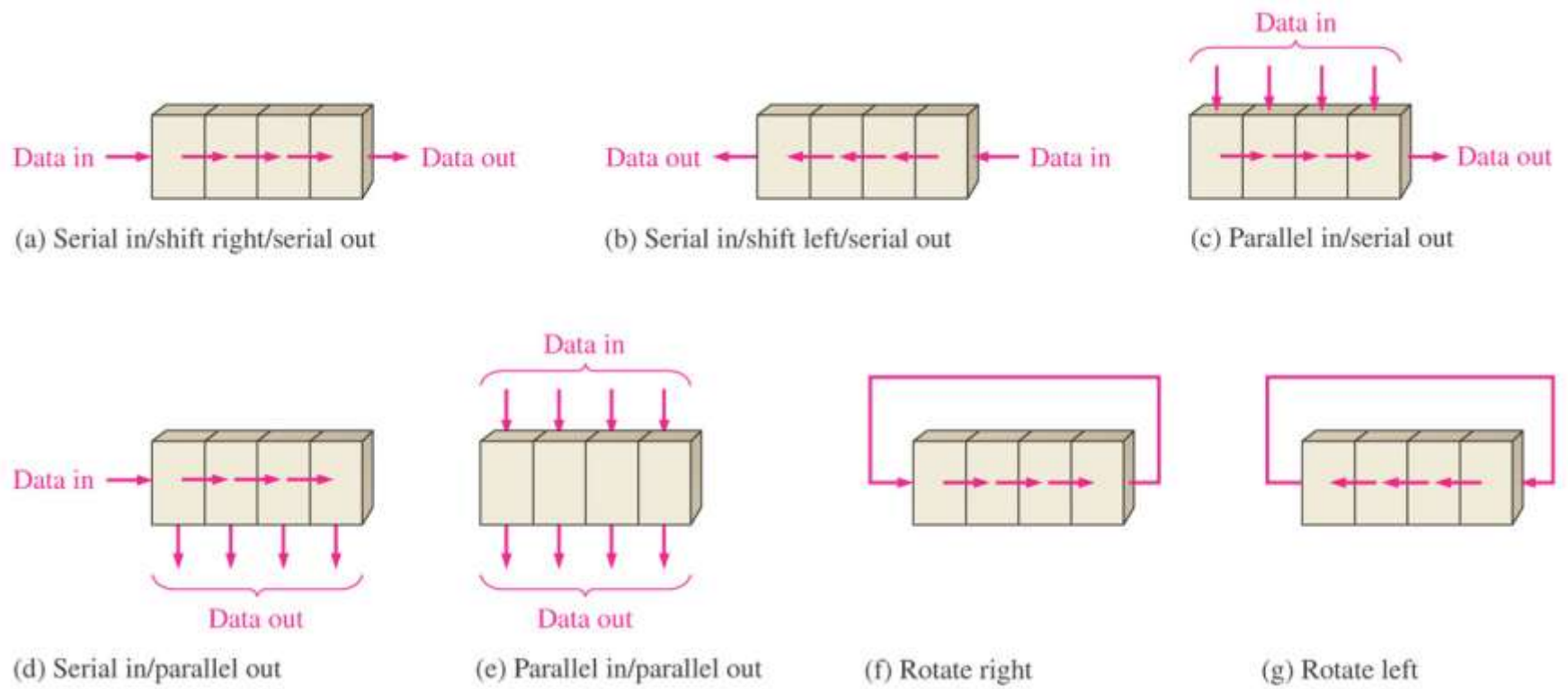



Figure 9-2 Basic data movement in shift registers. (Four bits are used for illustration. The bits move in the direction of the arrows.)

9.2 Serial IN/Serial OUT Shift Registers

- Accepts data serially
 - One bit at a time on a single line
 - Produces the stored information on its output also in serial form


Figure 9–3 Serial in/serial out shift register.

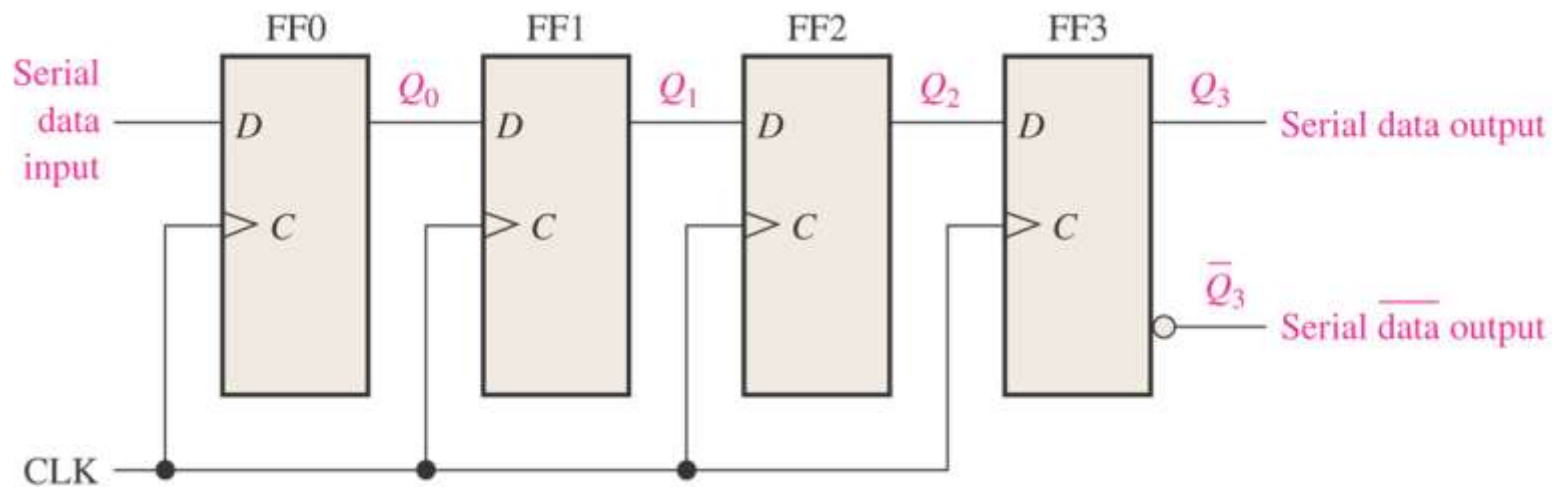

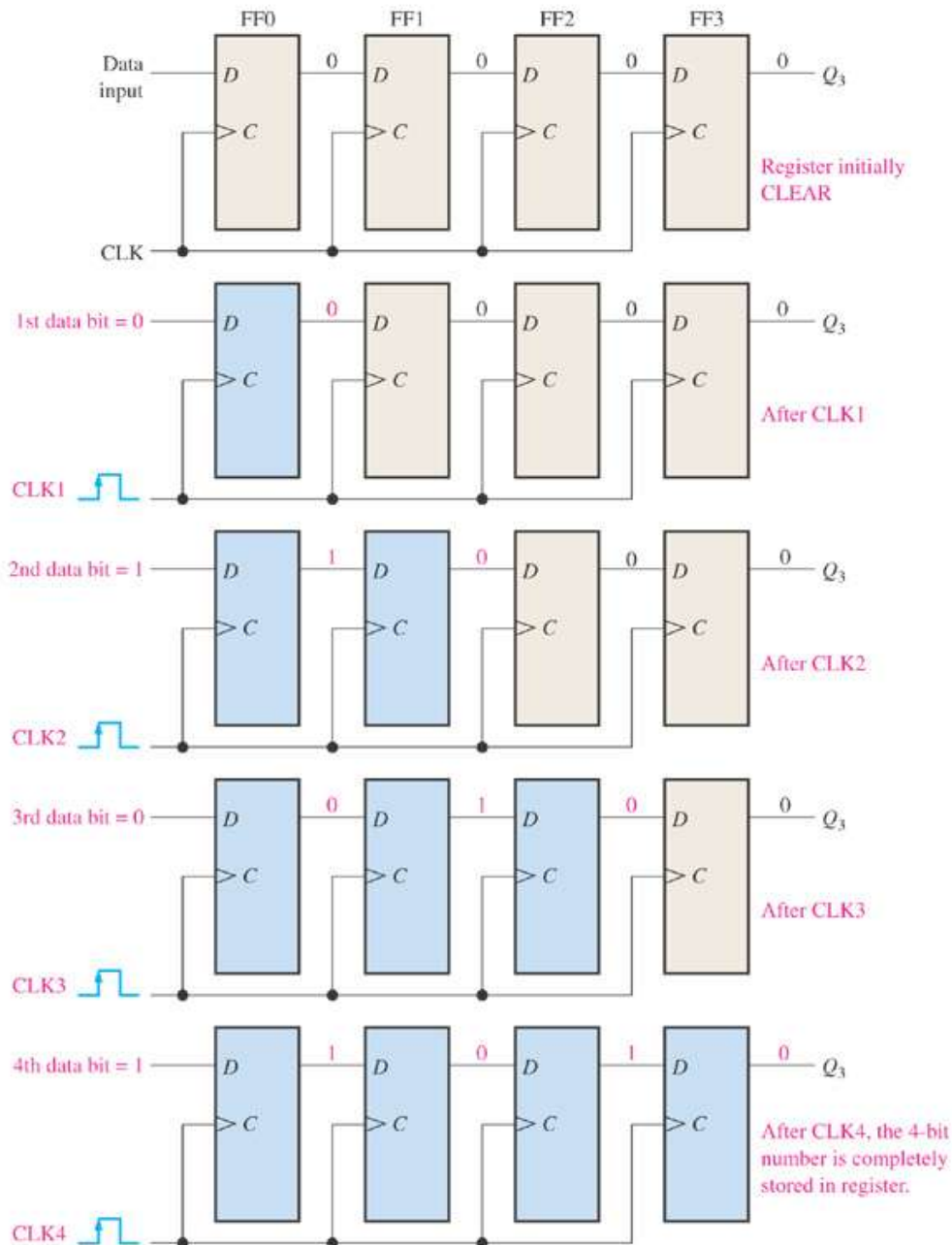

Four bits (1010) being entered serially into the register

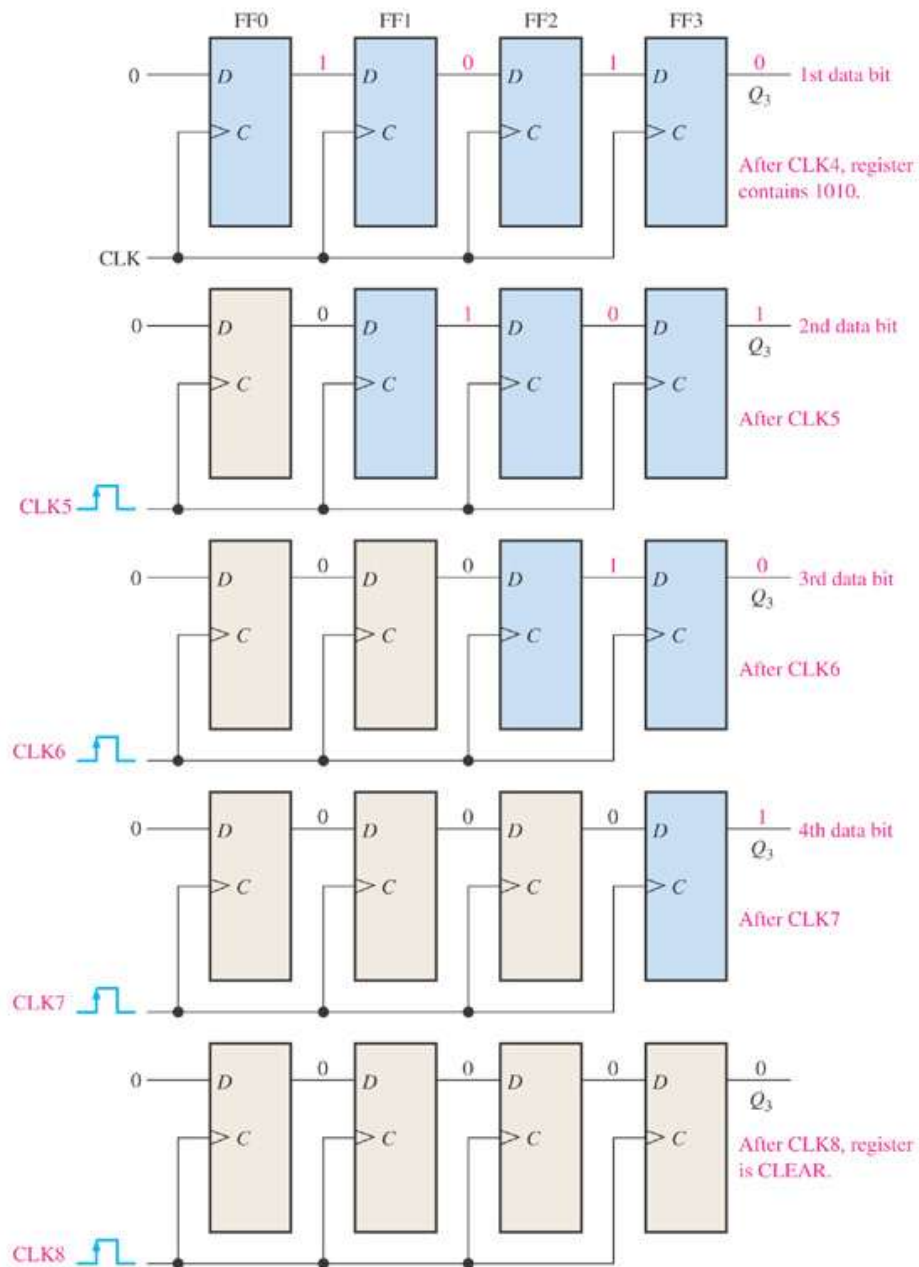Four bits (1010) being serially shifted out of the register and replaced by all zeros



Example: Show the states of the 5-bit register in Fig. 9-6(a) for the specified data input and clock waveform. Assume that the register is initially cleared.



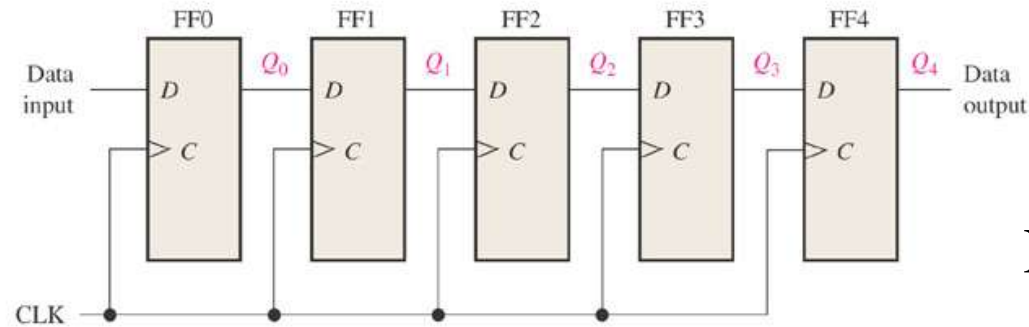


Fig. 9-6(a)

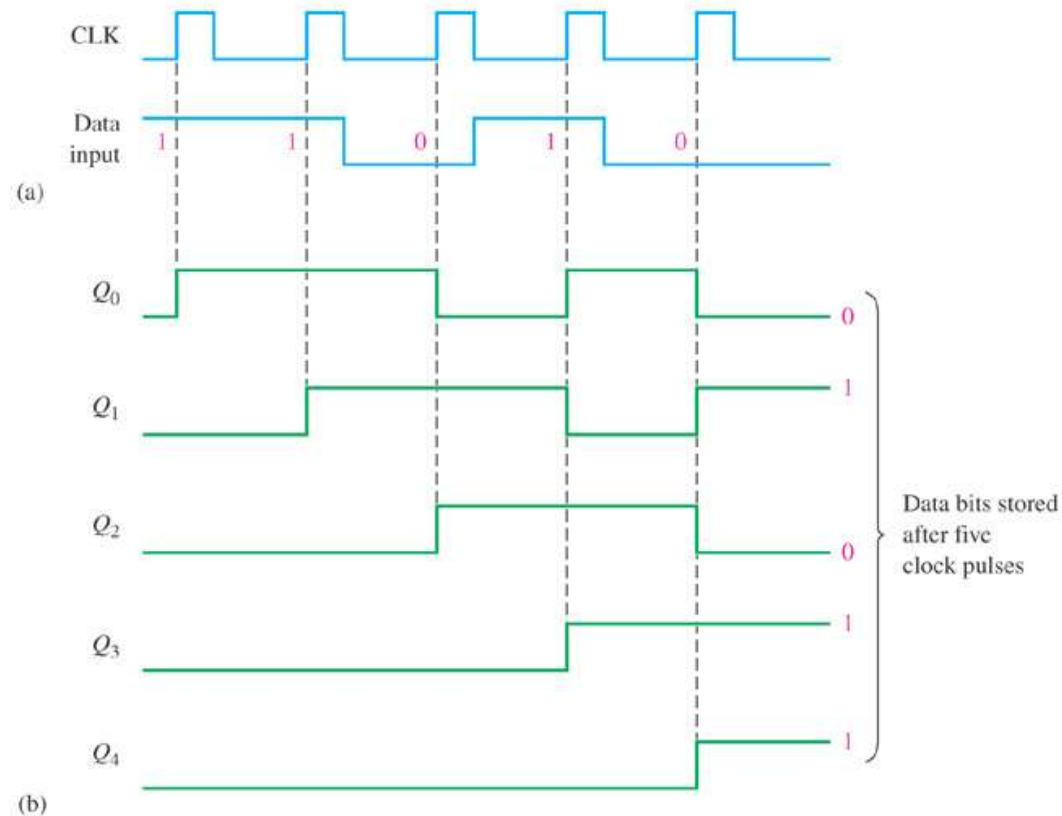


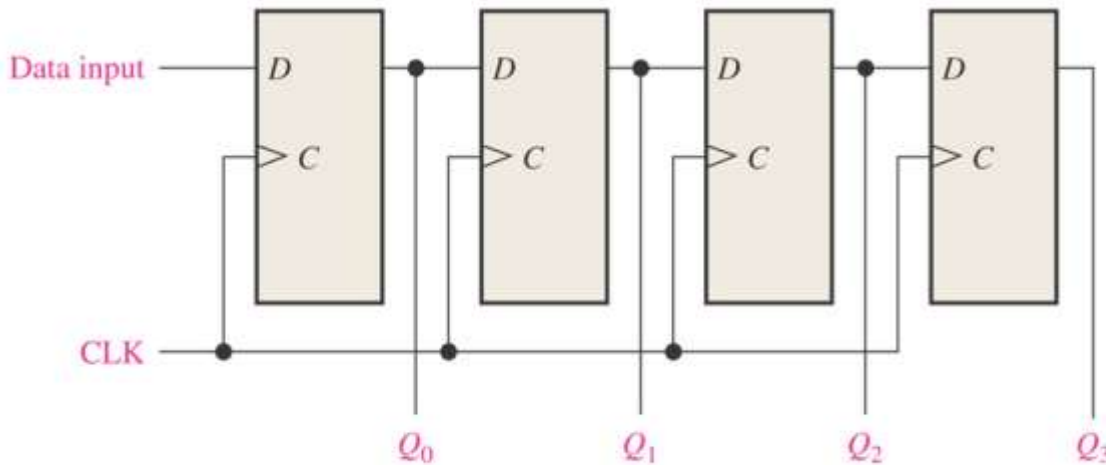9.3 Serial IN/Parallel OUT Registers

- Data bits enter into registers serially
- Data bits are taken out of the registers in the parallel way




(a)

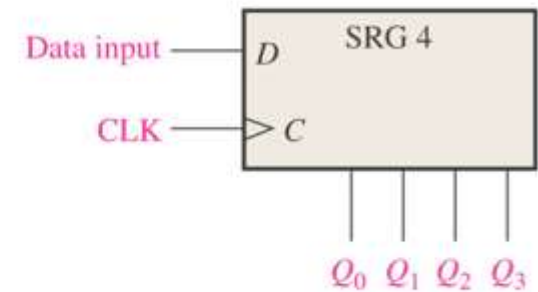


(b)

Figure 9–10 The 74HC164 8-bit serial in/parallel out shift register.

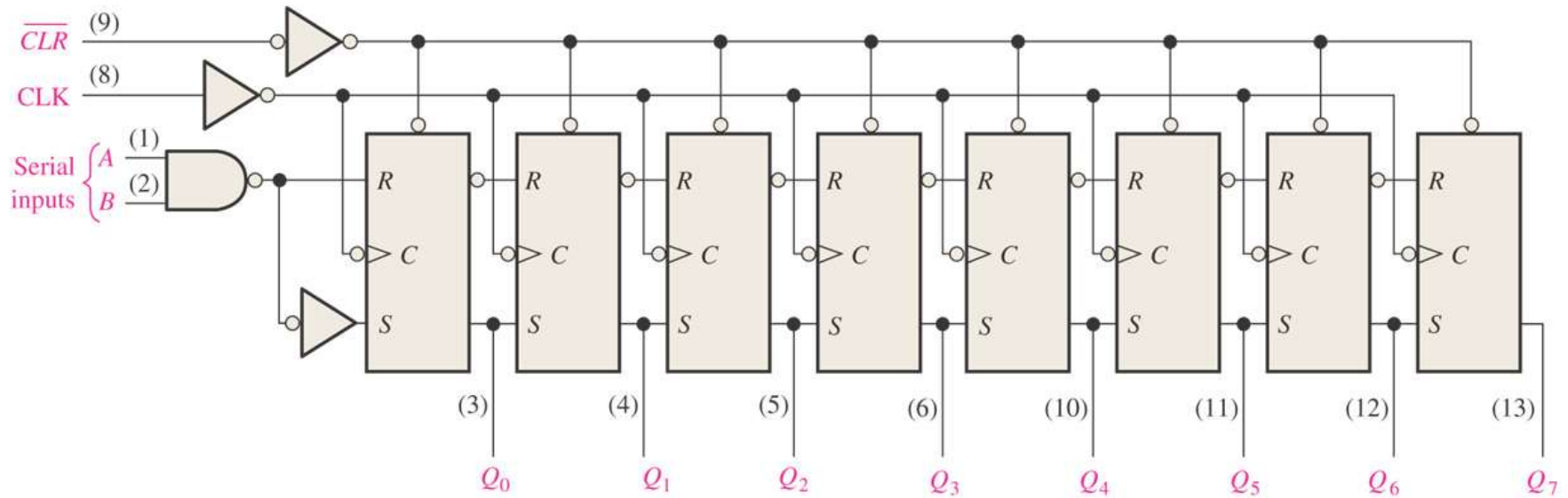


(a) Logic diagram

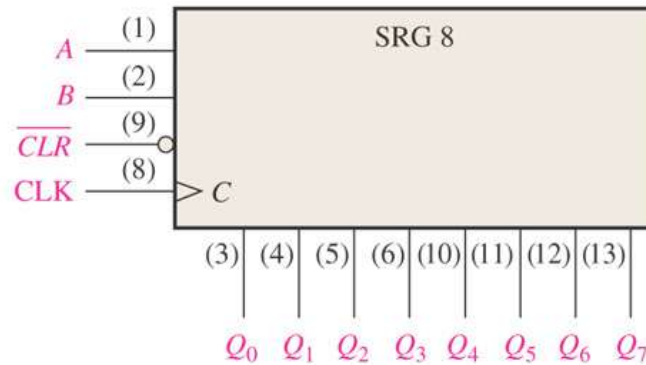

(b) Logic symbol


Figure 9–11 Sample timing diagram for a 74HC164 shift register.

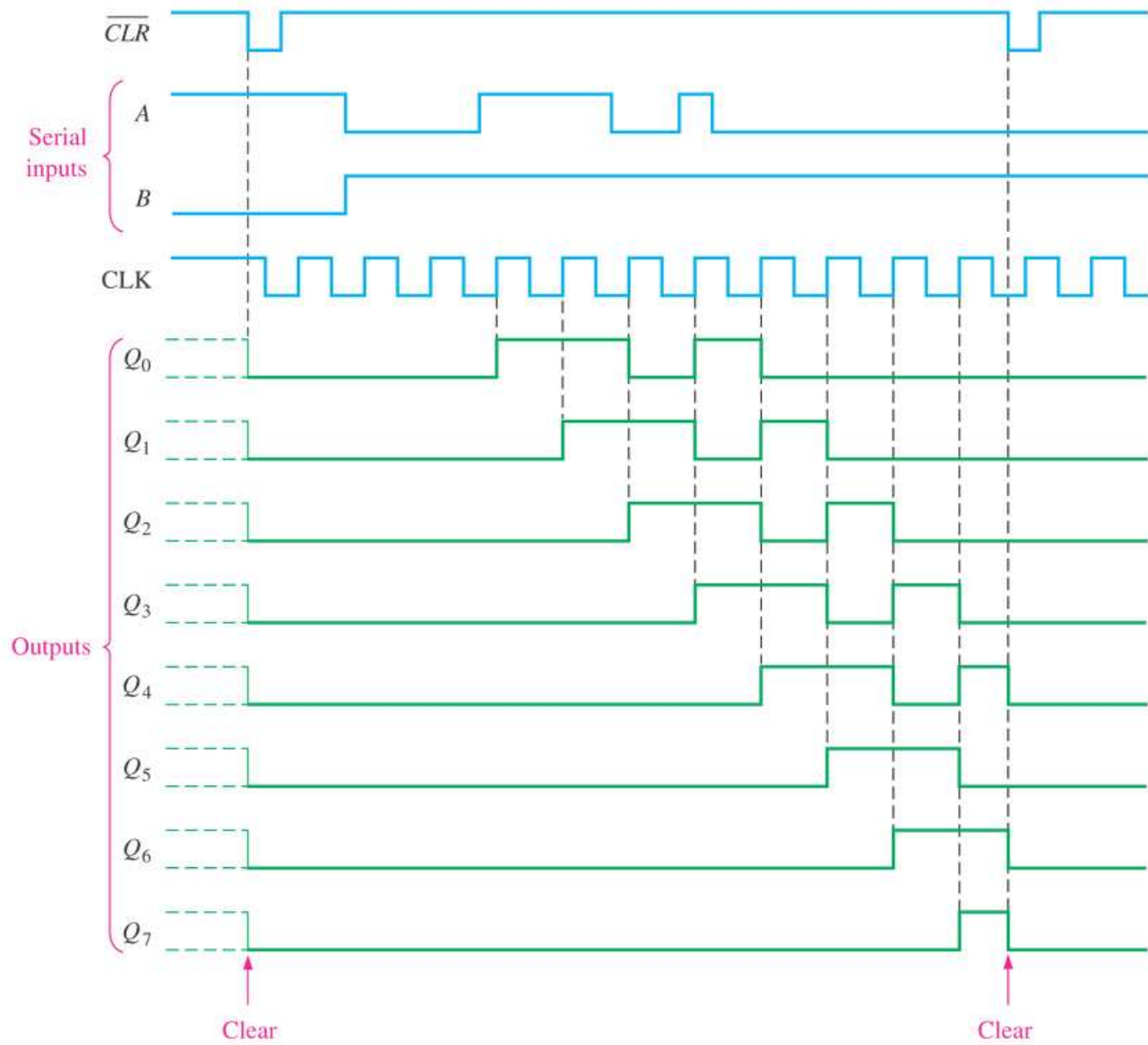


9.4 Parallel IN/Serial OUT Shift Registers

- Parallel inputs
- Serial outputs

Figure 9–12 A 4-bit parallel in/serial out shift register.

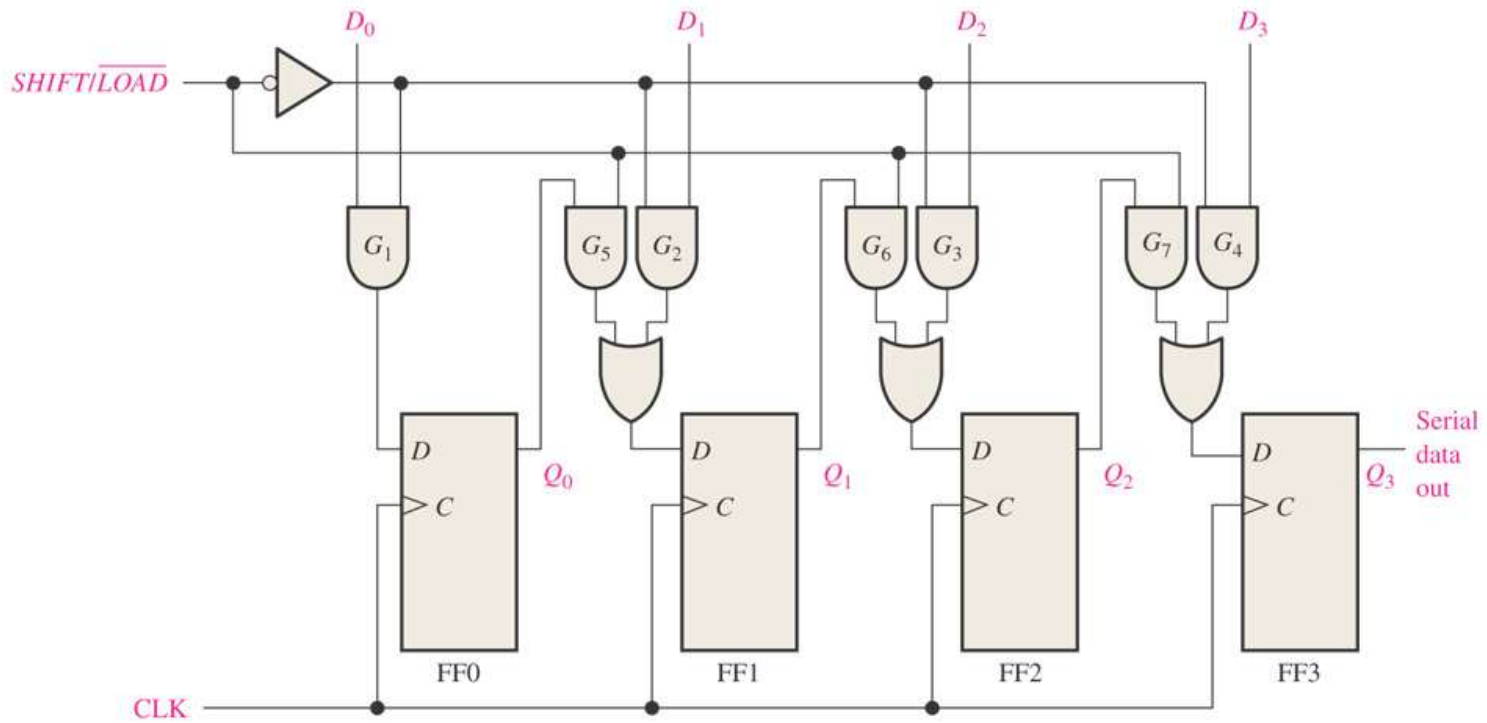


(a) Logic diagram

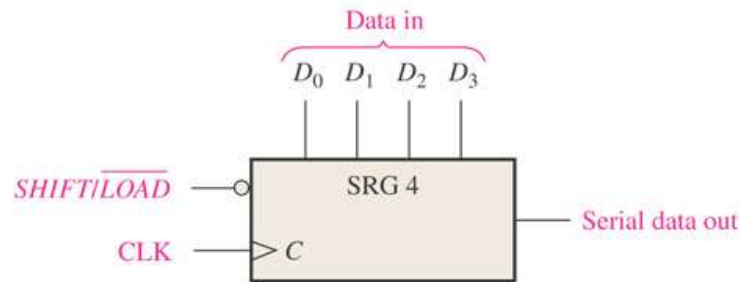


(b) Logic symbol

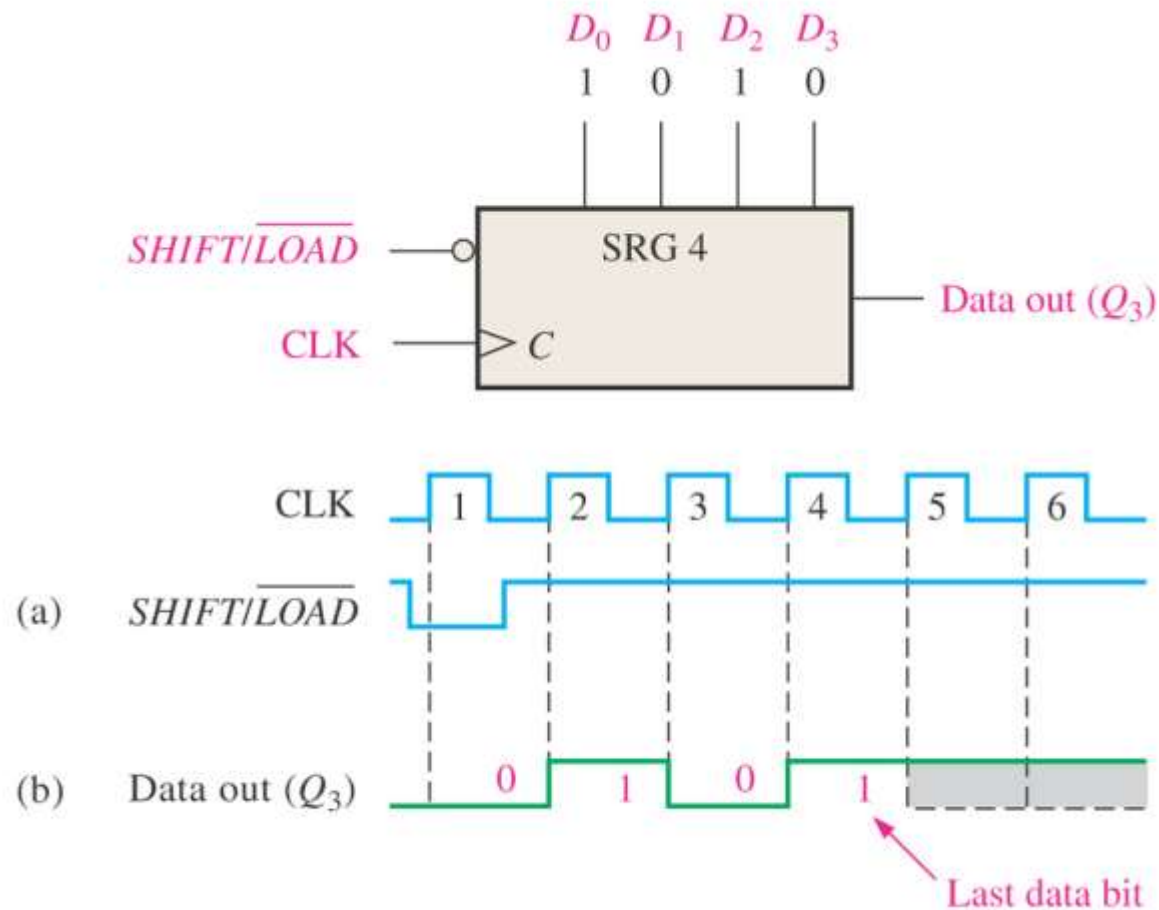Example: Show the data-output waveform for a 4-bit register with the parallel input data and the clock and other control signal.



9.5 Parallel IN/Parallel OUT Registers

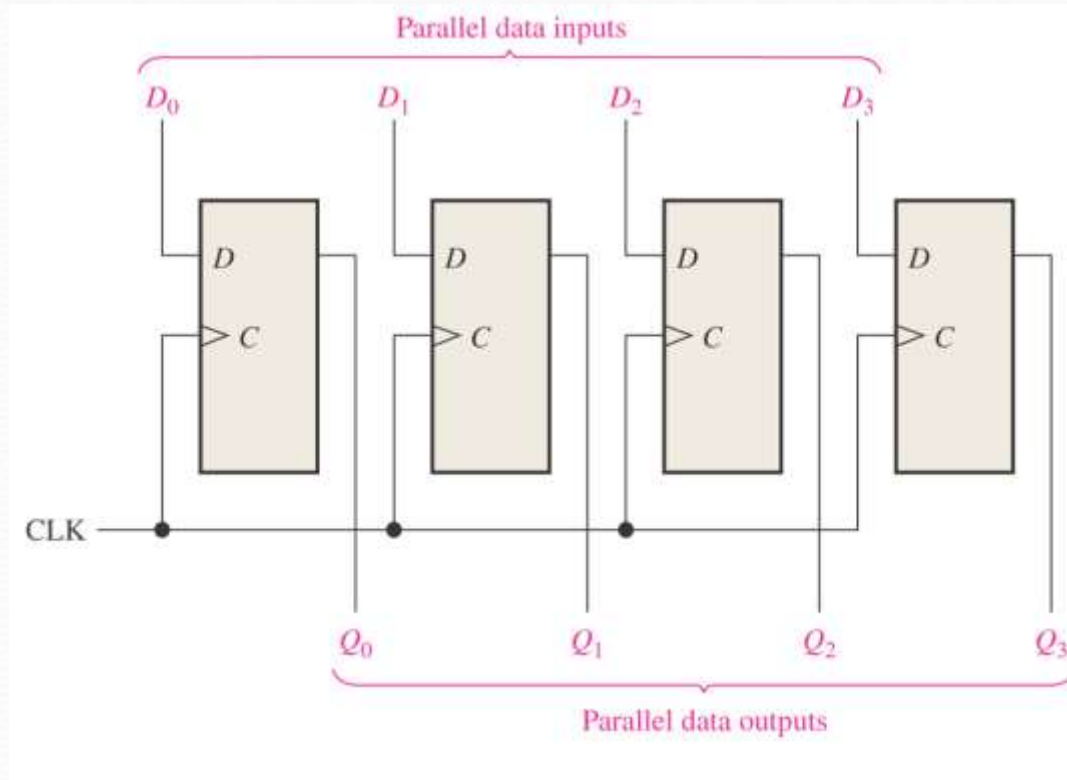

9.6 Bidirectional Shift Registers



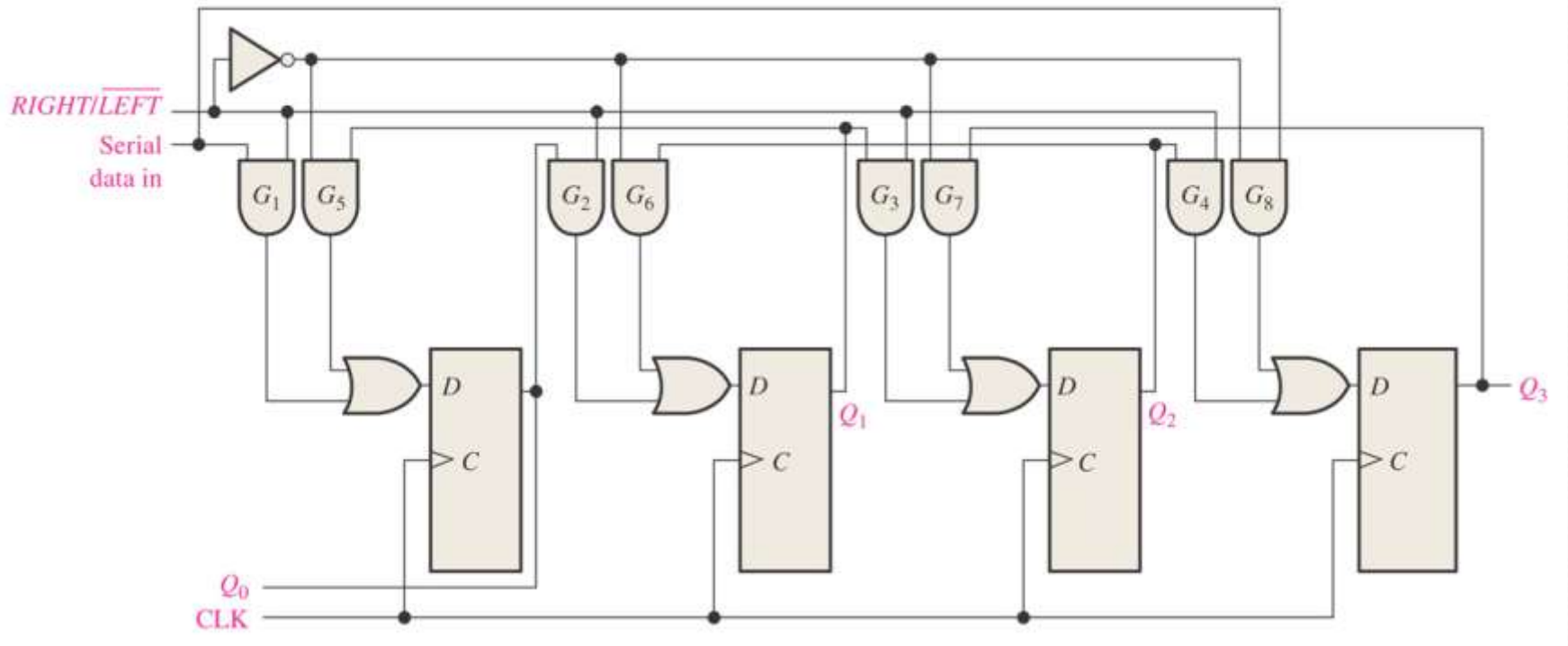


Fig. 9-19 Four-bit bidirectional shift register

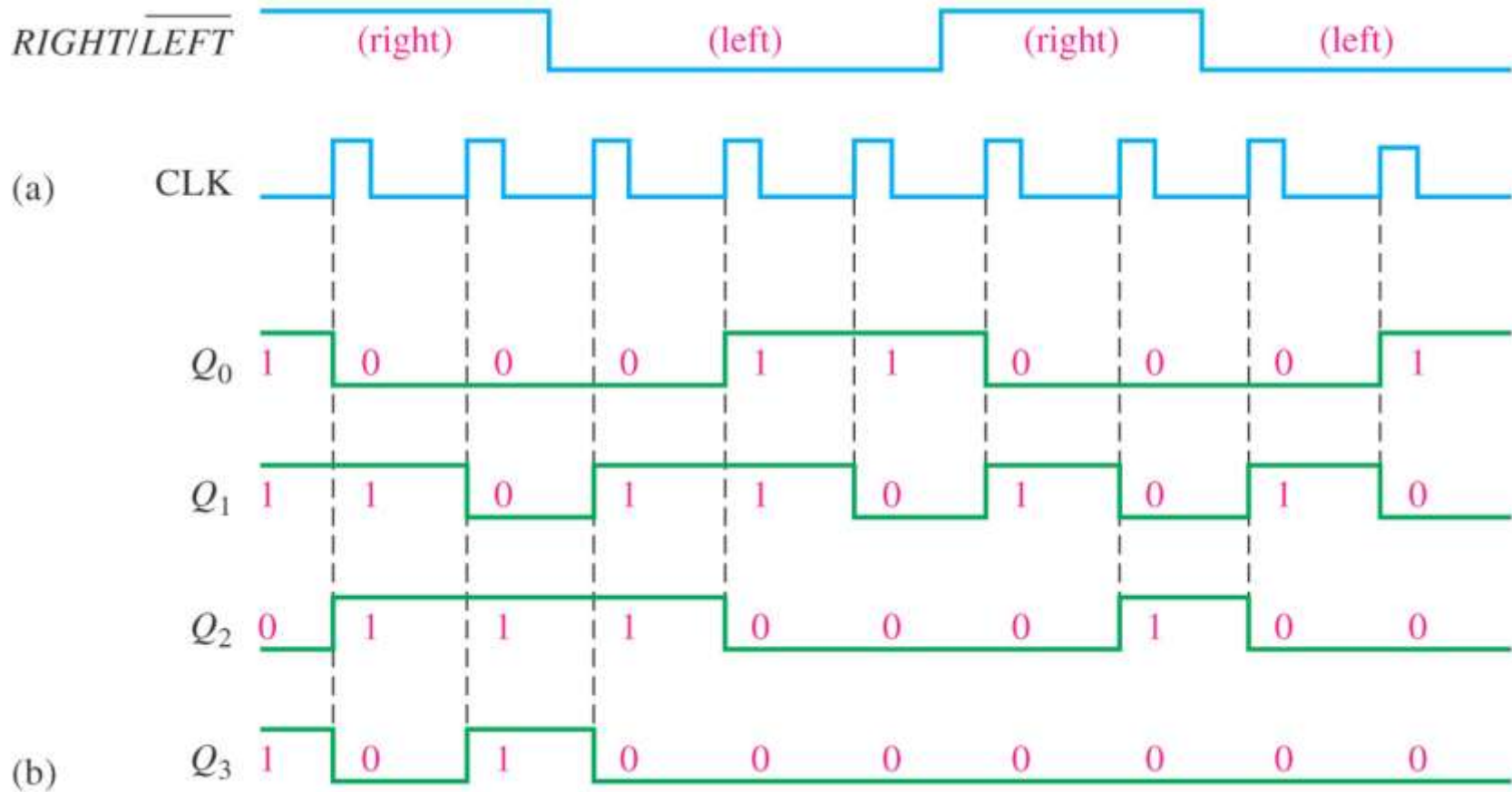
Example: Determine the state of the shift register of Fig. 9-19 after each clock pulse for the given control signals. Assume that the serial data-input line is LOW.



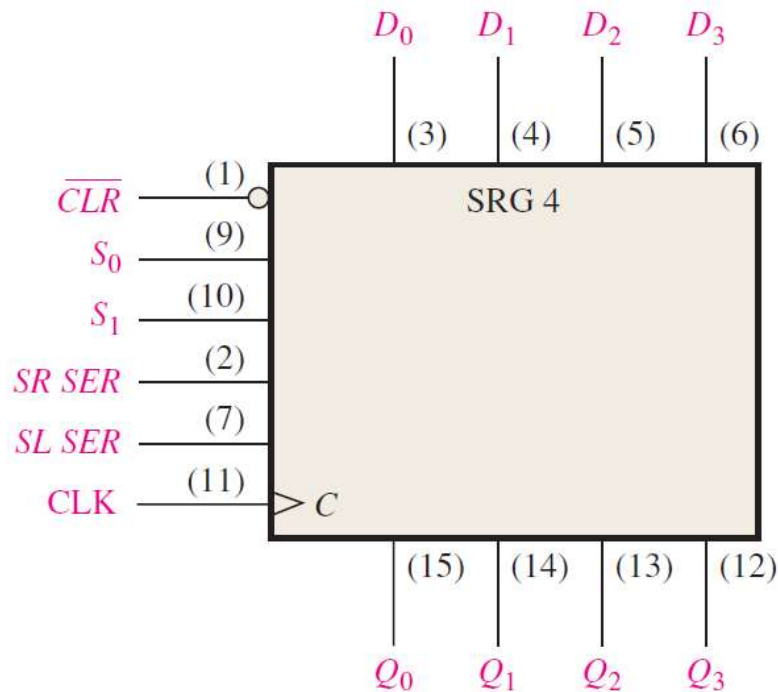The 74HC194 4-bit bidirectional universal shift register



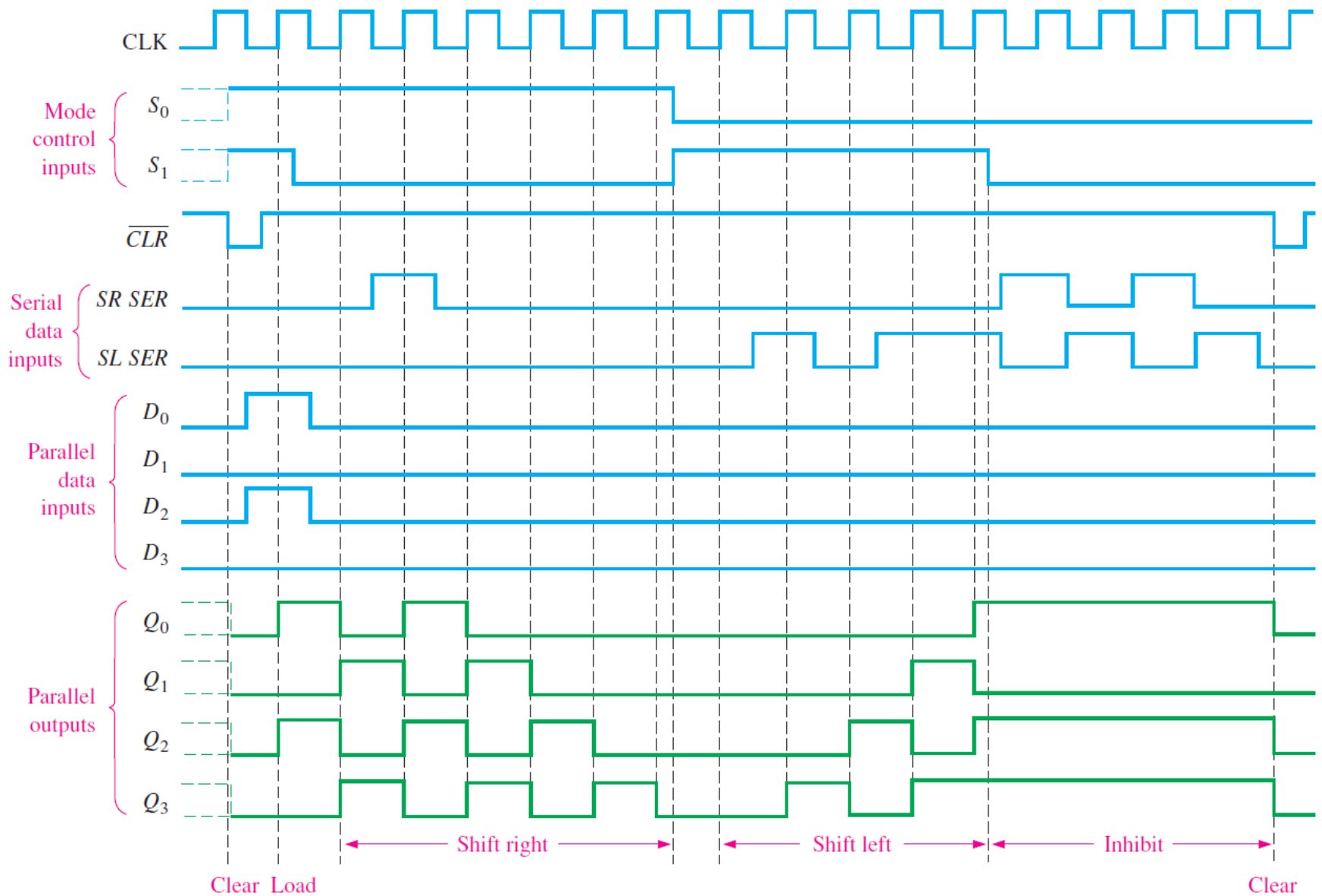- $S_0=S_1=1$: Data Preset
- $S_0=1, S_1=0$: Shift Right, Input from $SR\ SER$
- $S_0=0, S_1=1$: Shift Left, Input from $SL\ SER$
- $S_0=S_1=0$: Inhibit




Sample timing diagram for a 74HC194 shift register


9.7 Shift Register Counters

- The Johnson Counter
- The Ring Counter

Figure 9–23 Four-bit and 5-bit Johnson counters.

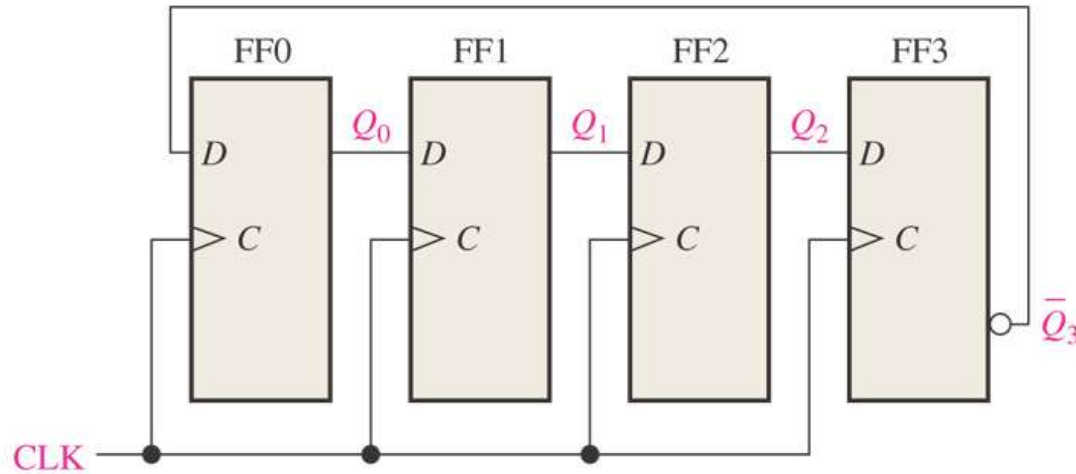

(a) Four-bit Johnson counter

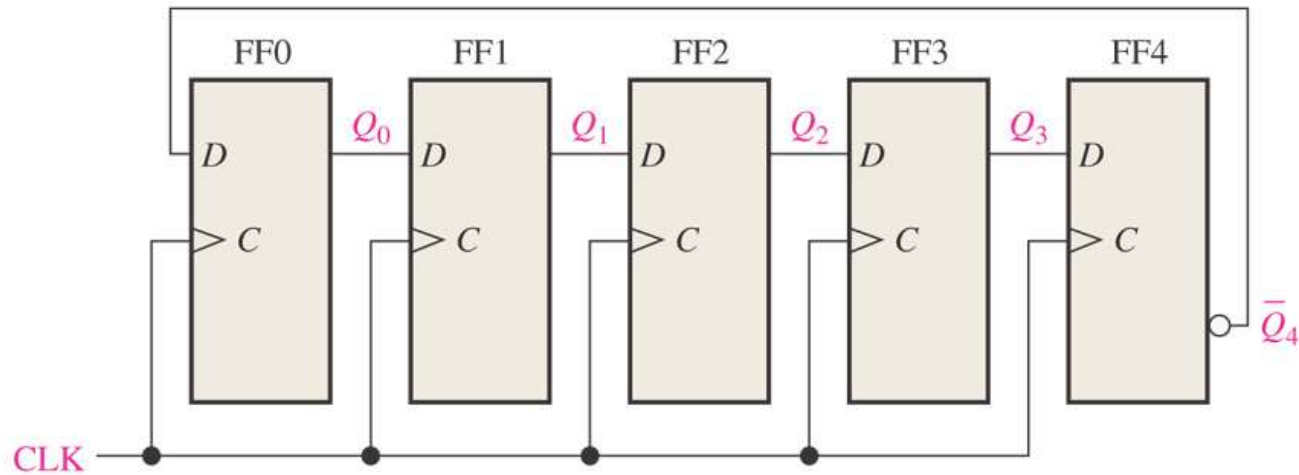

(b) Five-bit Johnson counter

Four-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

$$M=2N$$

Five-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1

Figure 9–24 Timing sequence for a 4-bit Johnson counter.

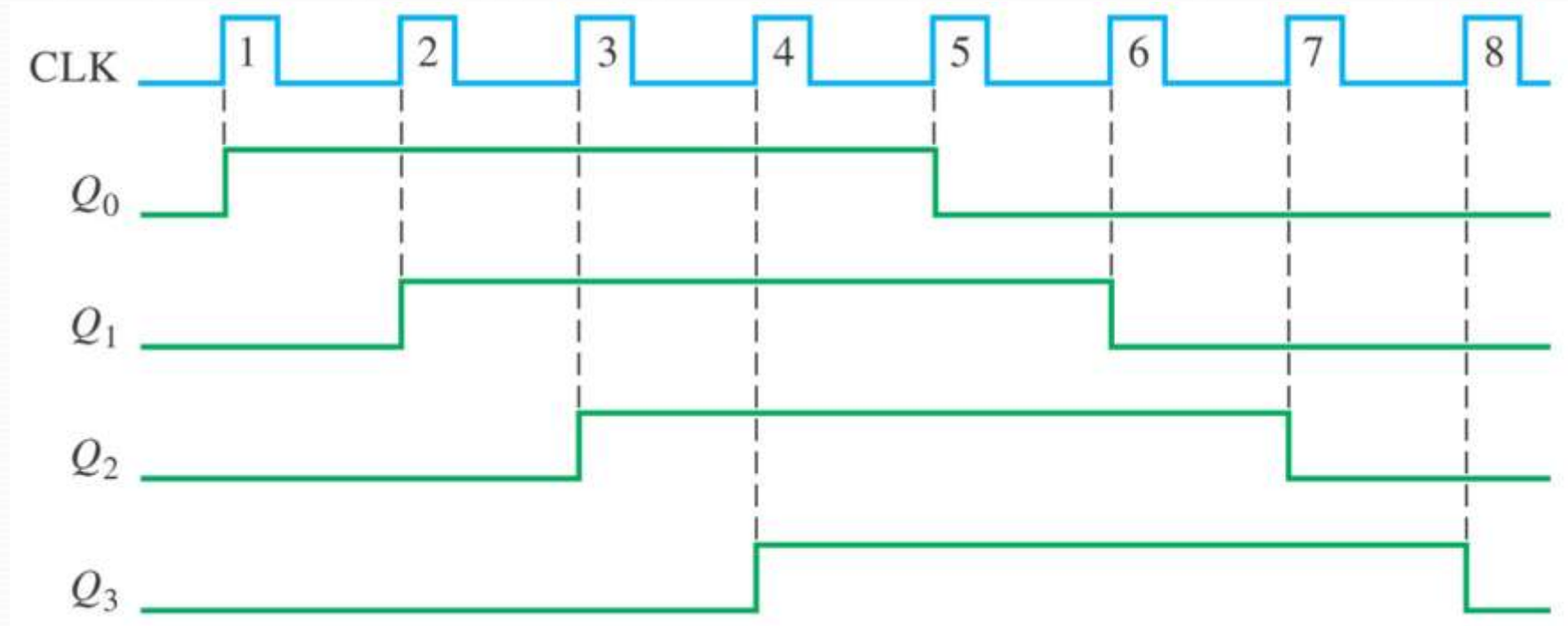


Figure 9–25 Timing sequence for a 5-bit Johnson counter.


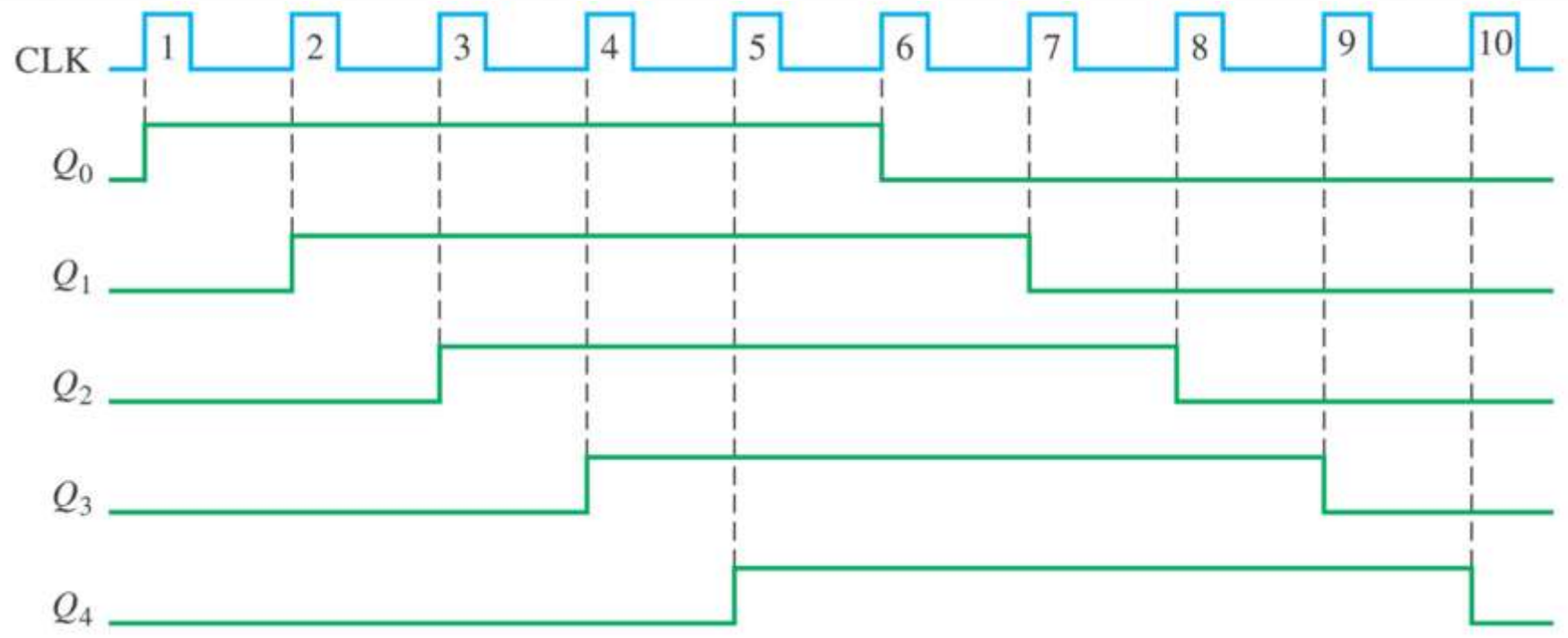


Figure 9–26 A 10-bit ring counter.

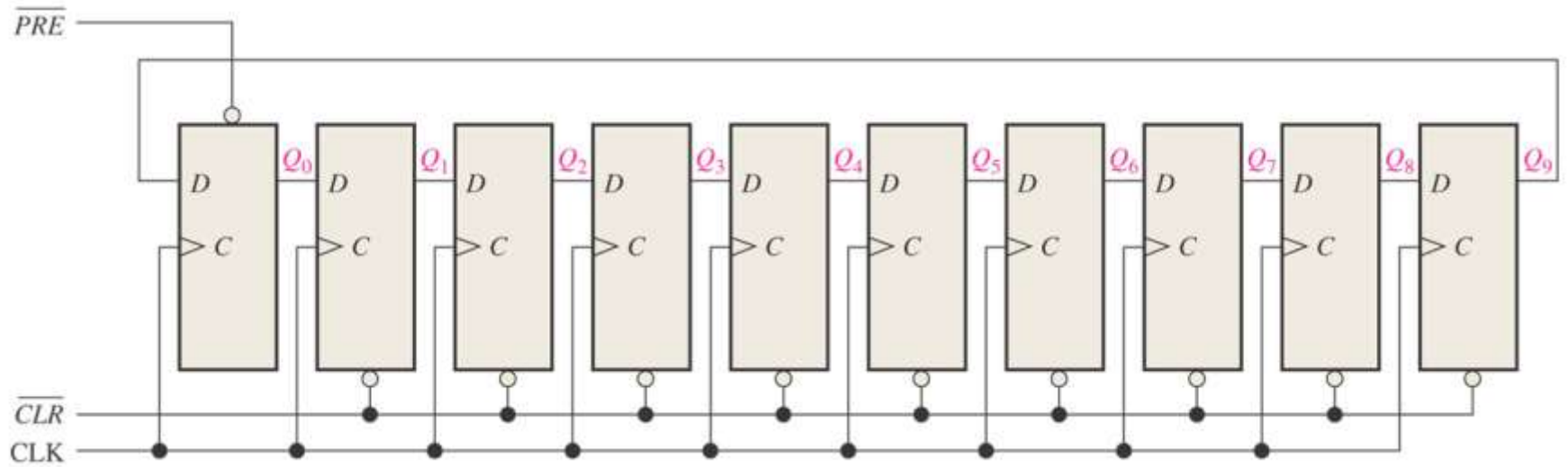


When the counter is initially set to 1000000000:

Ten-bit ring counter sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1


$M=N$

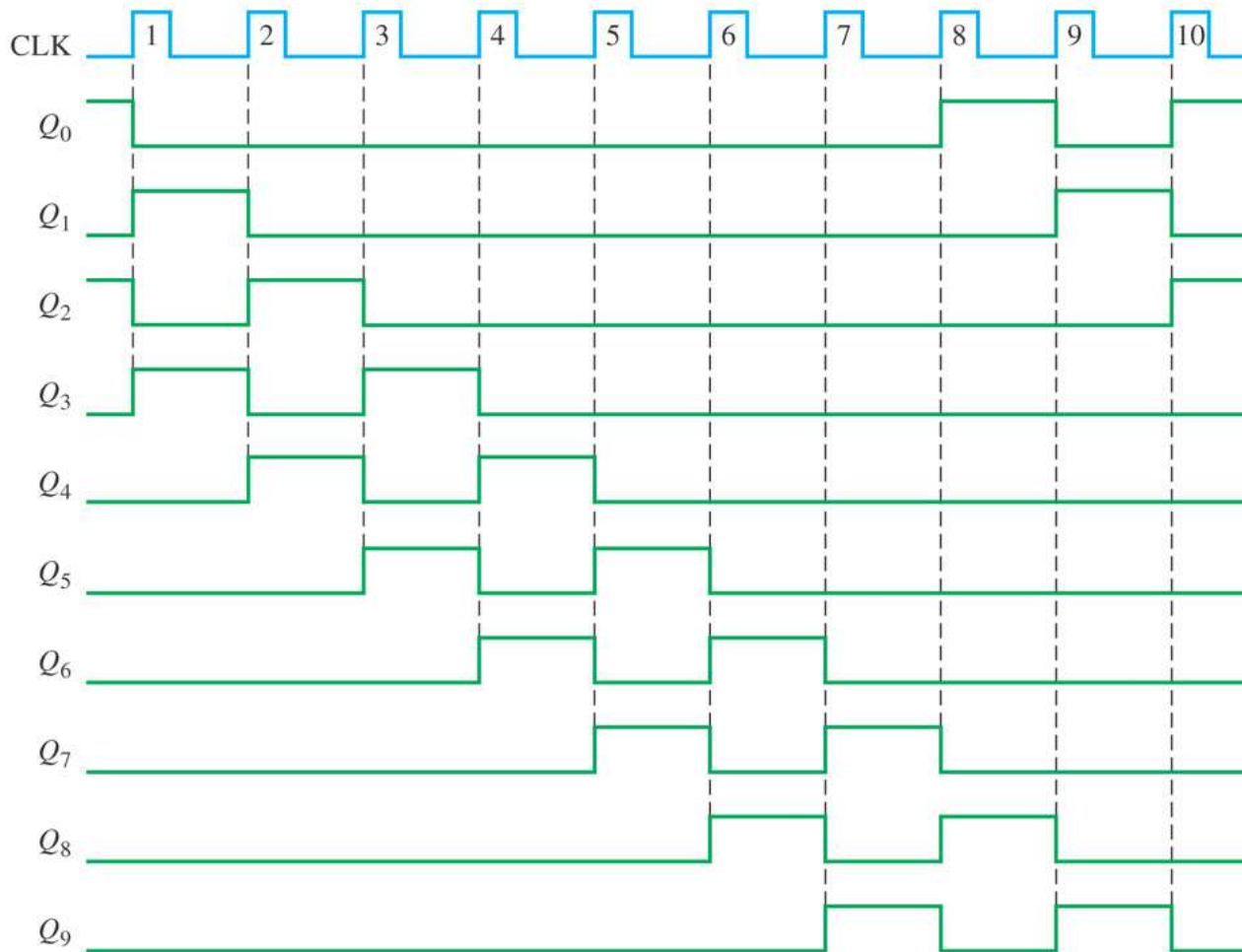When the counter is initially set to 0000000101:






9.8 Shift Register Applications

- Time delay


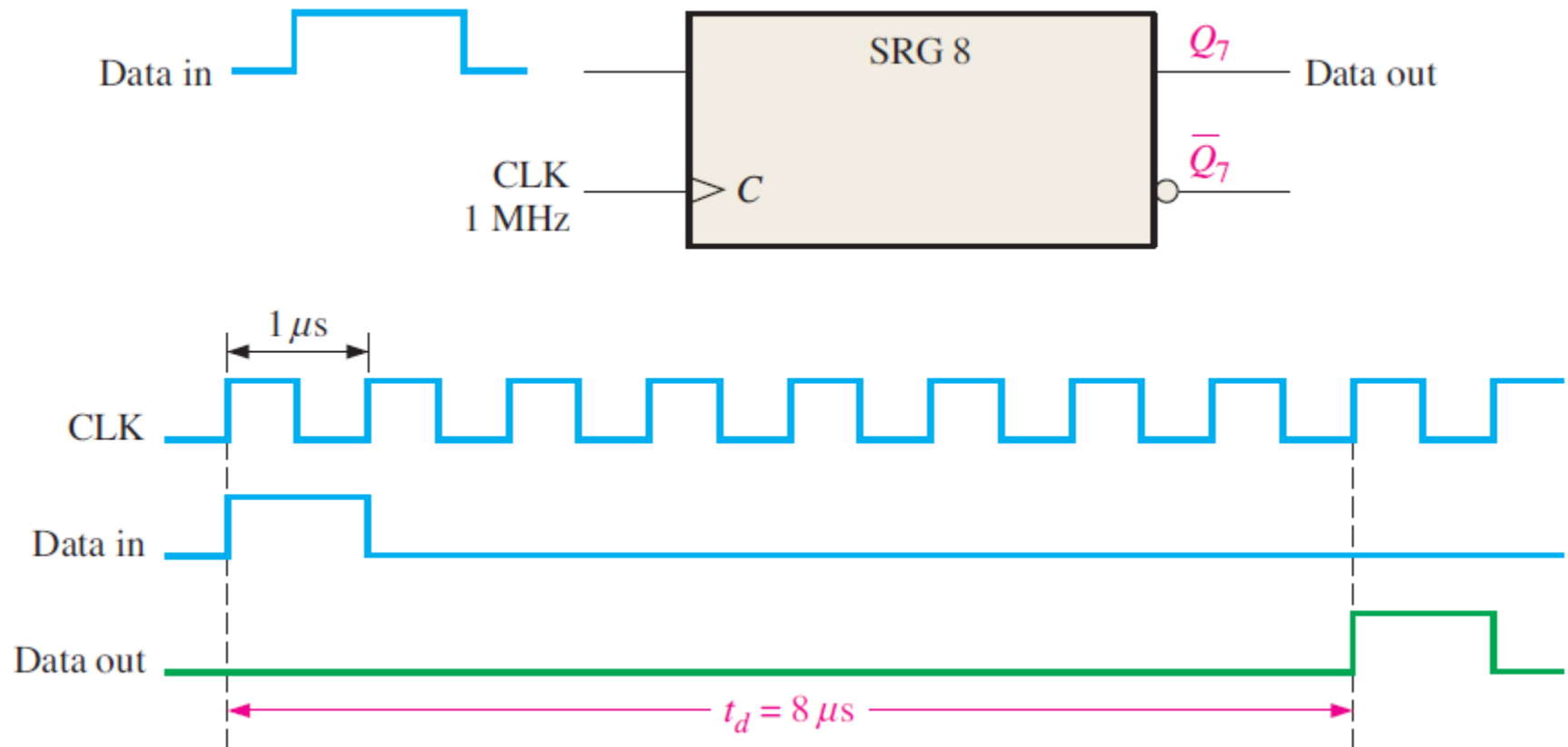


Serial to parallel data converter

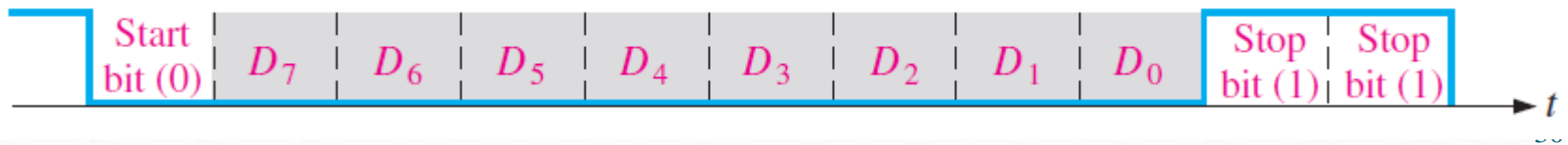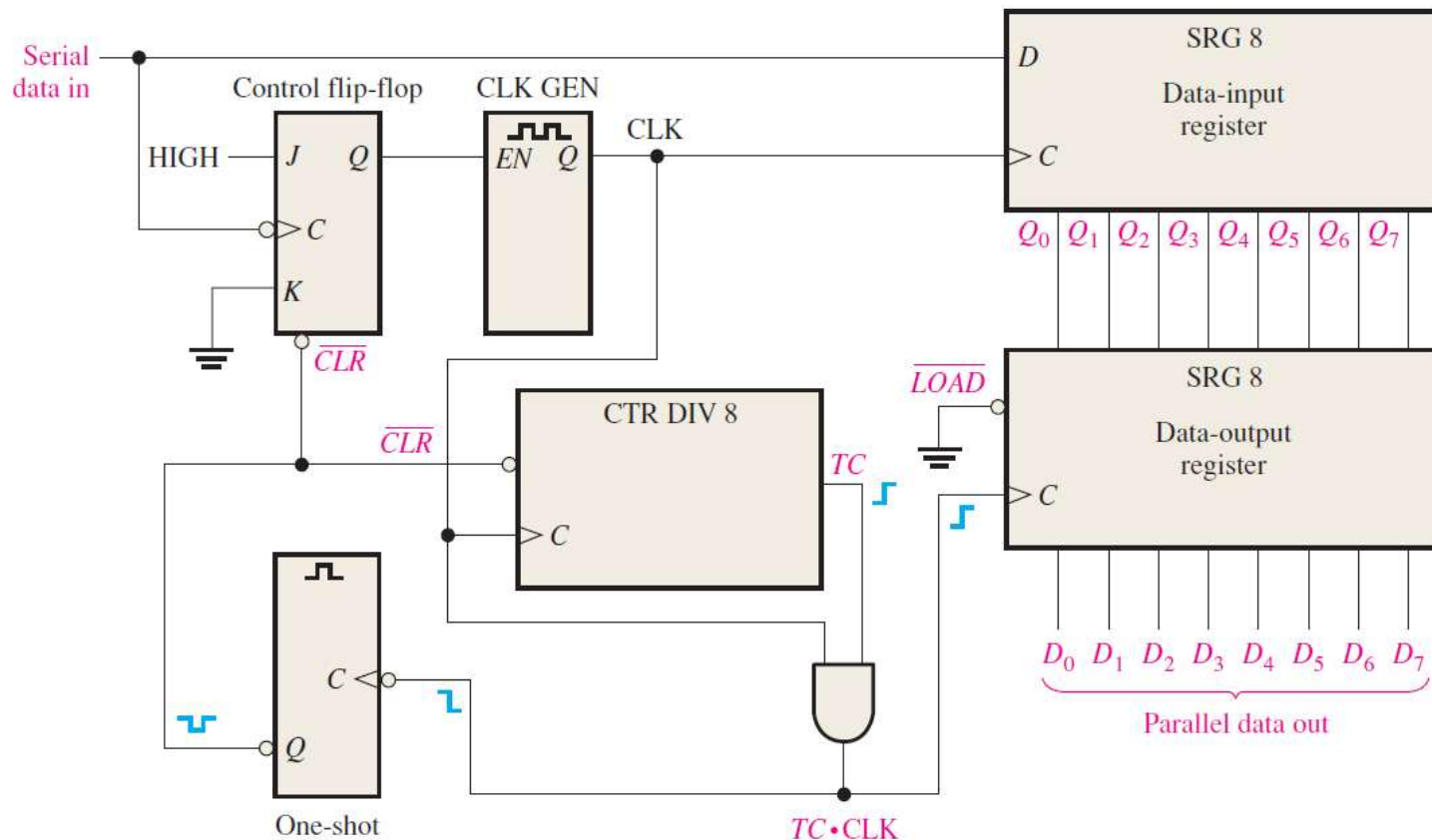

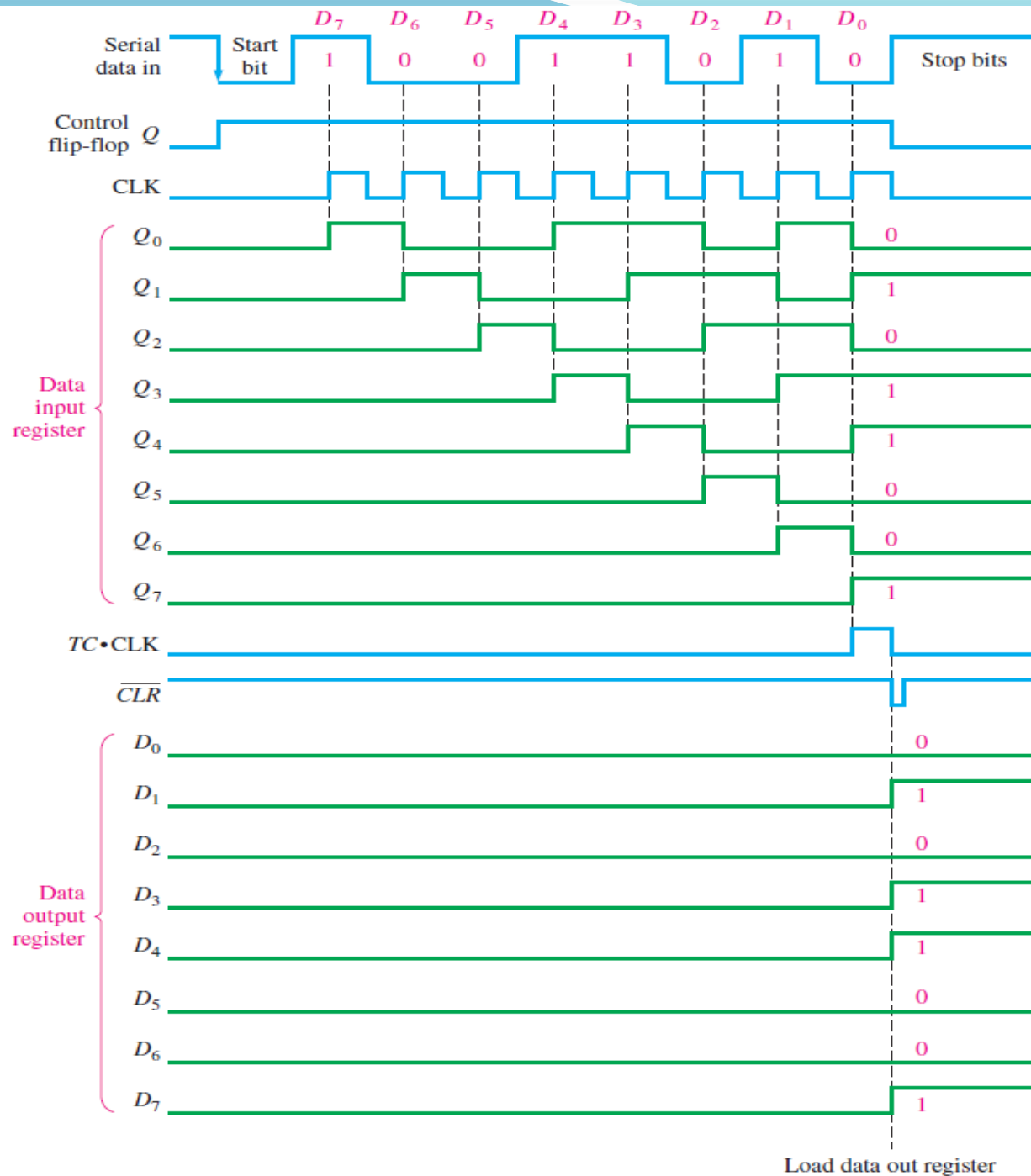

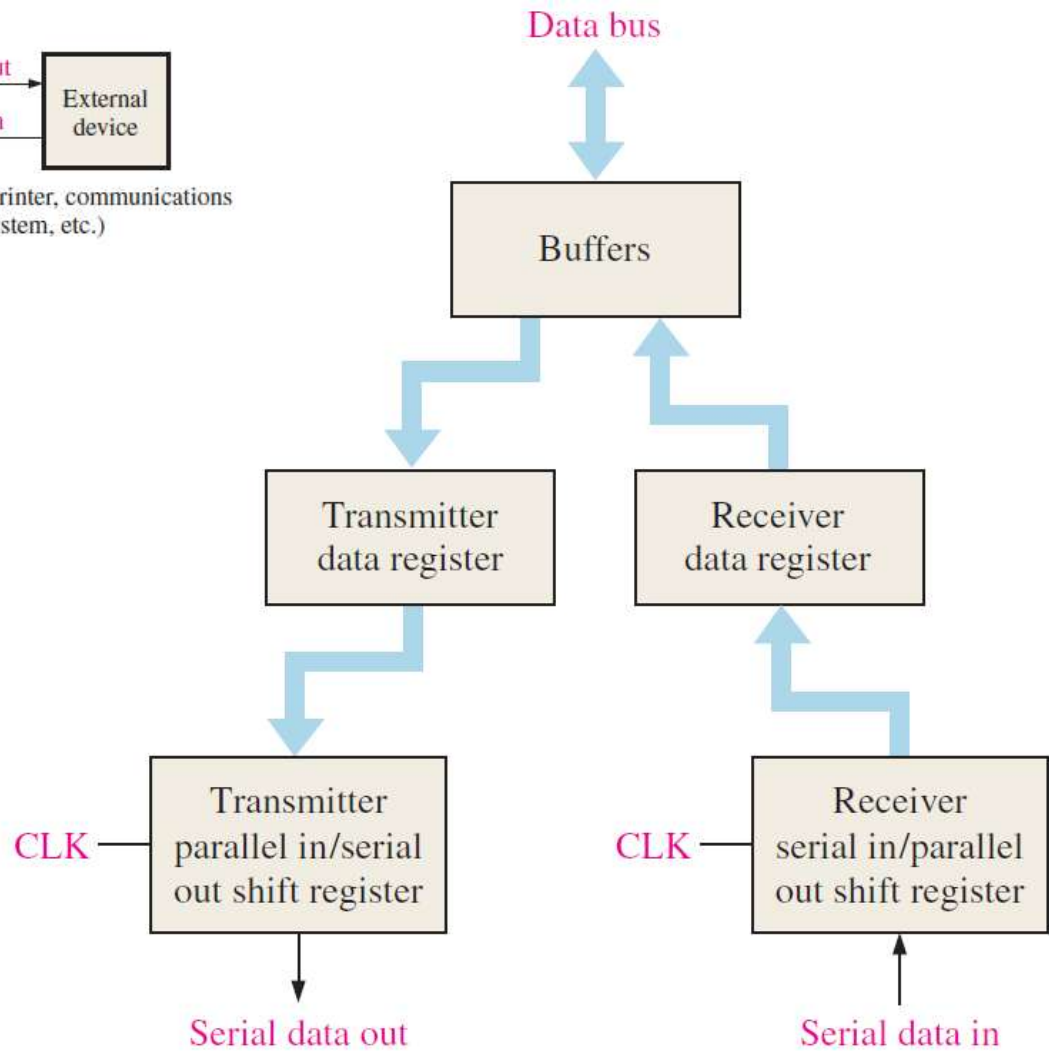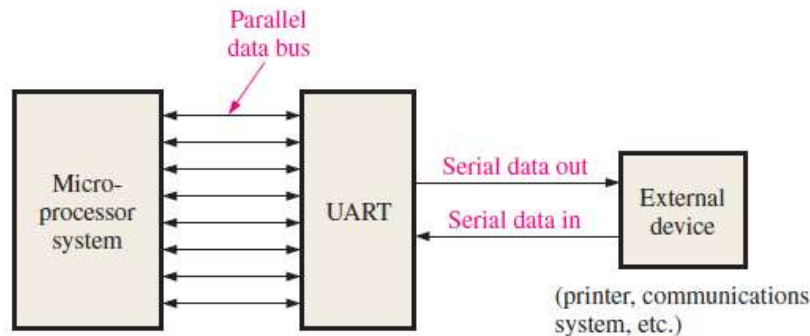Universal Asynchronous Receiver Transmitter (UART)



Summary

- The concept of shift register
- Some kinds of shift register
 - Serial In/Serial Out
 - Serial In/parallel Out
 - Parallel In/Serial Out
 - Parallel In/Parallel Out
 - Bidirectional Shift
- Shift register counters
- Applications

Assignments

- 10th Page 360

- 21
- 25

- 11th Page 286

- 21
- 25